

IV- Trouver la valeur des tensions manquantes: [10]

On donne:

$U_1 = 2 \text{ V}$

$U_8 = 6 \text{ V}$

$U_{\text{pile}} = 30 \text{ V}$

$U_2 = 3 \text{ V}$

$U_{10} = 2 \text{ V}$

$U_4 = 4 \text{ V}$

$U_{17} = 8 \text{ V}$

$U_6 = 3 \text{ V}$

